

VESP Vision

To be the centre of excellence in the field of technical education.

Program Code:-AO2I,EE2I

Course Name:-Applied Science(Physics)

Course Code : -22211

Course coordinator: Mrs. Deepa Gupte

Date: 1/4/21



Unit No:1

Unit Name: Electricity and Capacitance

Unit Outcomes (UO1d): Explain concept of Wheatstone's bridge.

Learning Outcome (LO4) : Students will be able to explain principle of Wheatstone's bridge




- ▶ Students will be explain principle of Wheatstone's bridge



Wheatstone's Network

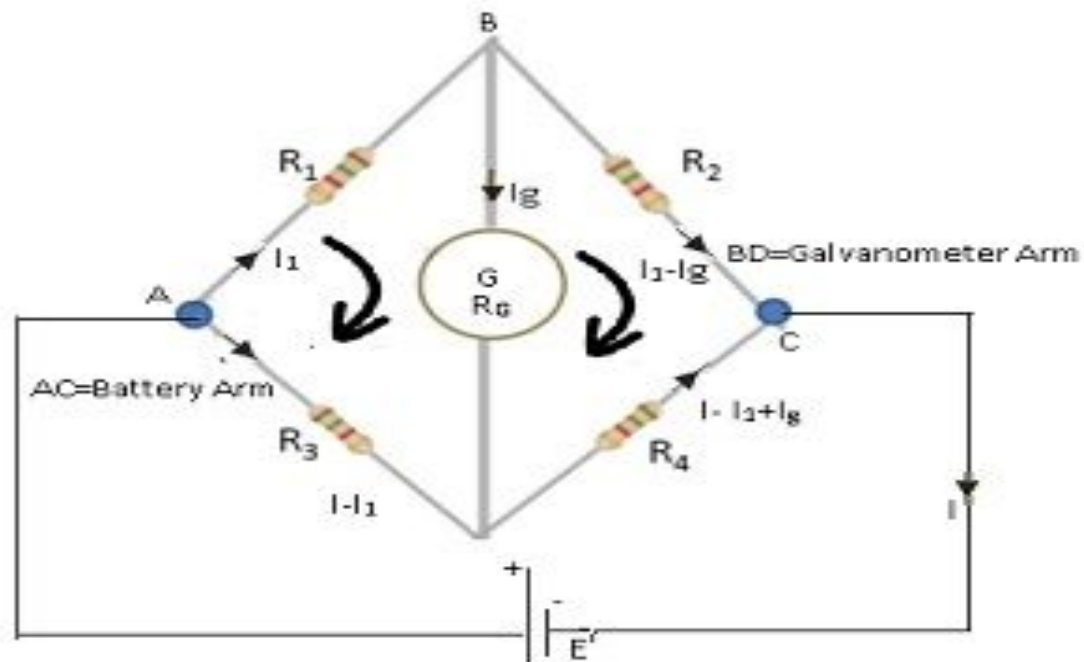- ▶ Wheatstone bridge is a special arrangement of resistors as shown in the figure.




- ▶ There are 4 resistances R_1, R_2, R_3 and R_4 arranged in such a manner that there is a galvanometer placed between the points B and D.
- ▶
- ▶ The arm BD is known as galvanometer arm. AC is known as battery arm.
- ▶
- ▶ And circuit is connected to the battery across the pair of diagonally opposite points A and C.
- ▶ According to Wheatstone bridge principle:-
 - ▶ If $(R_1/R_2)=(R_3/R_4)$, then Bridge is said to be balanced.
 - ▶ If the bridge is balanced there is no current flowing through the galvanometer arm.

- ▶ Mathematically:-
- ▶ Assume current across the galvanometer arm $I_g = 0$;
- ▶ To prove:- $(R_1/R_2) = (R_3/R_4)$
- ▶ Applying loop law to the loop ABDA,
- ▶ There is no Emf, therefore,
- ▶ $0 = I_1 R_1 - (I - I_1) R_3 + I_g R_g$ equation (i) where R_g = resistance of galvanometer.
- ▶ Applying loop Law to the loop BCDB,
- ▶ No Emf, $0 = (I_1 - I_g) R_2 - (I - I_1 + I_g) R_4 + I_g R_g$ equation(ii)
- ▶ Putting $I_g = 0$ in equation(i) and (ii)
- ▶ $I_1 R_1 - (I - I_1) R_3 = 0 \Rightarrow I_1 R_1 = (I - I_1) R_3$ equation (iii)
- ▶ $I_1 R_2 - (I - I_1) R_4 = 0 \Rightarrow I_1 R_2 = (I - I_1) R_4$ equation(iv)
- ▶ Dividing equation(iii) with (iv)
- ▶ **$(R_1/R_2) = (R_3/R_4)$ Hence proved.**

- The Wheatstone bridge is used for the precise measurement of low resistance.
- Wheatstone bridge along with operational amplifier is used to measure physical parameters such as temperature, light, and strain.
-

Meter Bridge

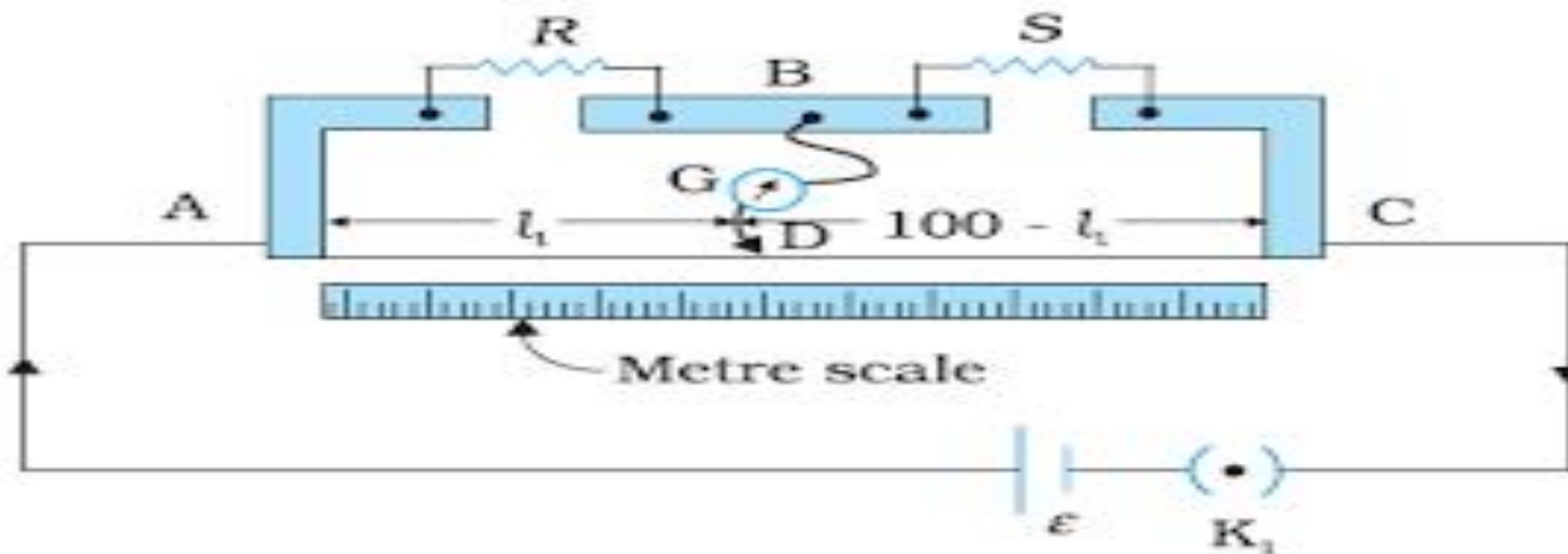A **meter bridge** also called a slide wire **bridge** is an instrument that works on the principle of a Wheatstone **bridge**. A **meter bridge** is used in finding the unknown resistance of a conductor as that of in a Wheatstone **bridge**.



Formula to determine unknown resistance by meter bridge



$$R_1/R_2 = R_3/R_4$$

Now can be written as

$$R/S = l_1/100 - l_1$$

If R is unknown

$$\text{then } R = S (l_1/100 - l_1)$$

Numerical on Wheatstone's bridge



Four resistances 4 ohm, 8 ohm, 6 ohm and x ohm are connected in a cyclic order so as to form Wheatstone's network. If the network is balanced, find the value of 'X'.

Solution: Given: $R_1 = 4 \text{ ohm}$, $R_2 = 8 \text{ ohm}$, $R_3 = 6 \text{ ohm}$ To find: Unknown resistance (X).

Formula: $R_1/R_2 = R_4/R_3$

$$4/8 = X/6$$

$$X = (4/8) \times 6$$

$$x = 3 \text{ Ohm}$$

Numerical on meter bridge



An unknown resistance 'X' is placed in the left gap and a known resistance of 60 ohm is placed in the right gap of a metre bridge. The null point is obtained at 70 cm from the left end of the bridge. Find the unknown resistance.

Solution: Given: $R = 60$, $l_1 = 70$ cm, $l_2 = 100 - 70 = 30$ cm To find: Unknown resistance (X) Formula: $X/R = l_1/l_2$

Calculation: From formula, $X/60 = 70/30$

$X = 140$ ohm

Ans: The unknown resistance is 140 ohm.