


# Kirchoff's Laws

# Circuit Definitions

- **Node** – any point where 2 or more circuit elements are connected together
  - Wires usually have negligible resistance
  - Each node has one voltage (w.r.t. ground)
- **Branch** – a circuit element between two nodes
- **Loop** – a collection of branches that form a closed path returning to the same node without going through any other nodes or branches twice


# Example

- How many nodes, branches & loops?

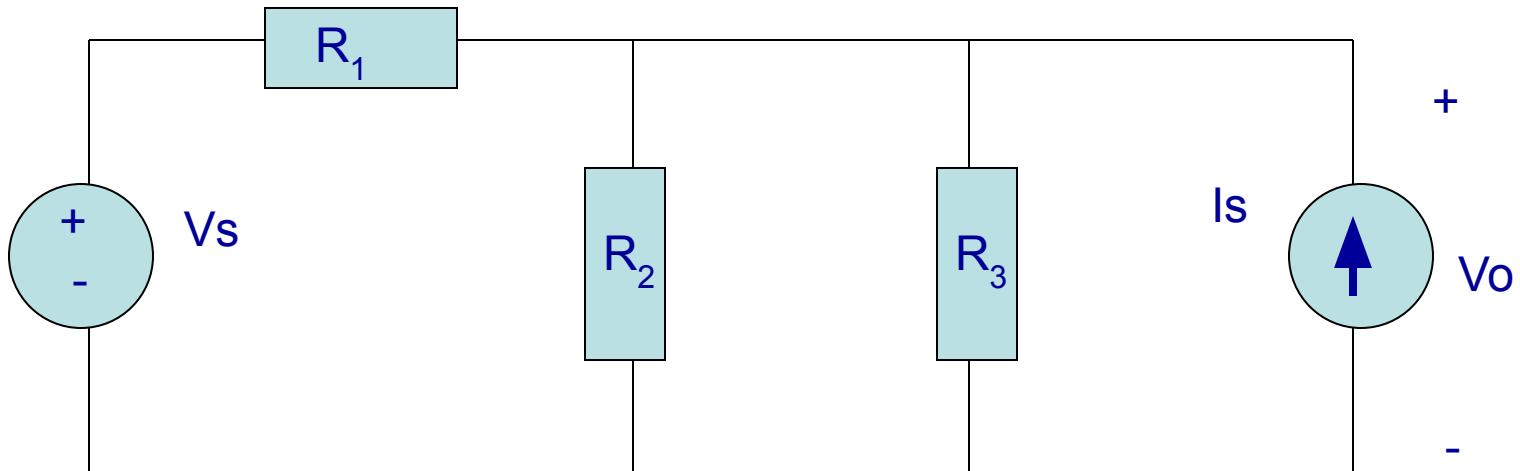


# Example

- Three nodes

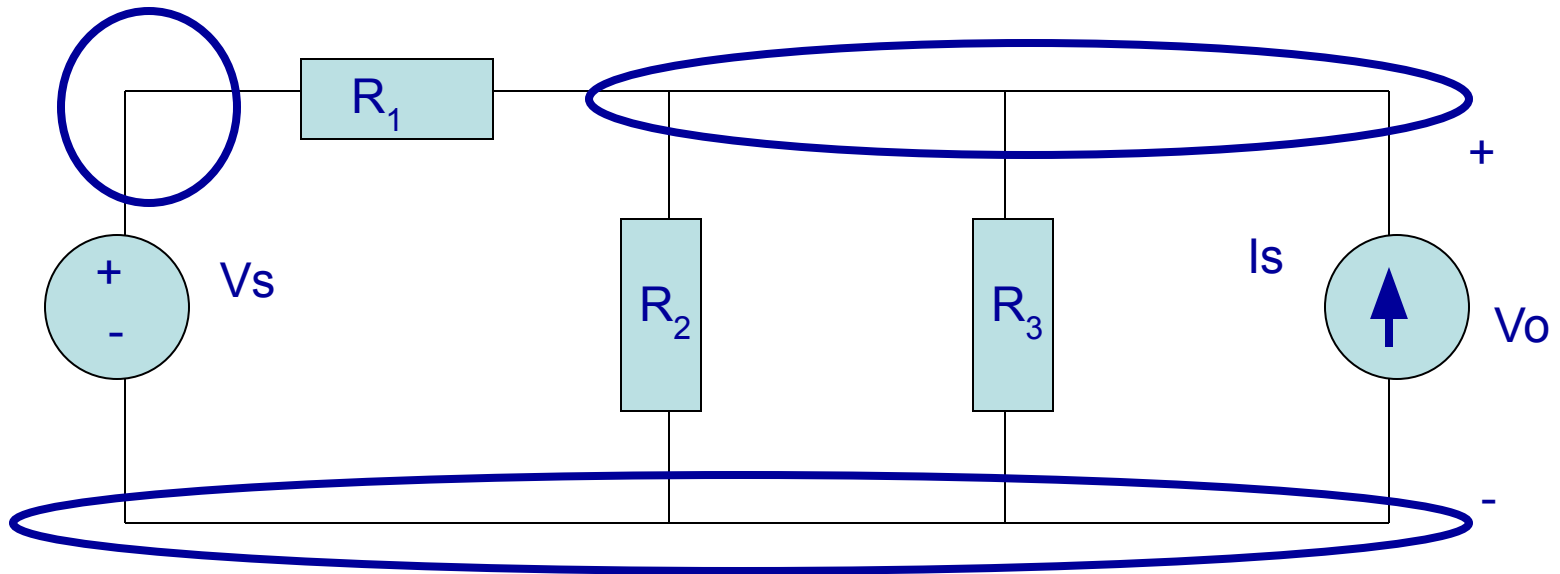


# Example

- 5 Branches

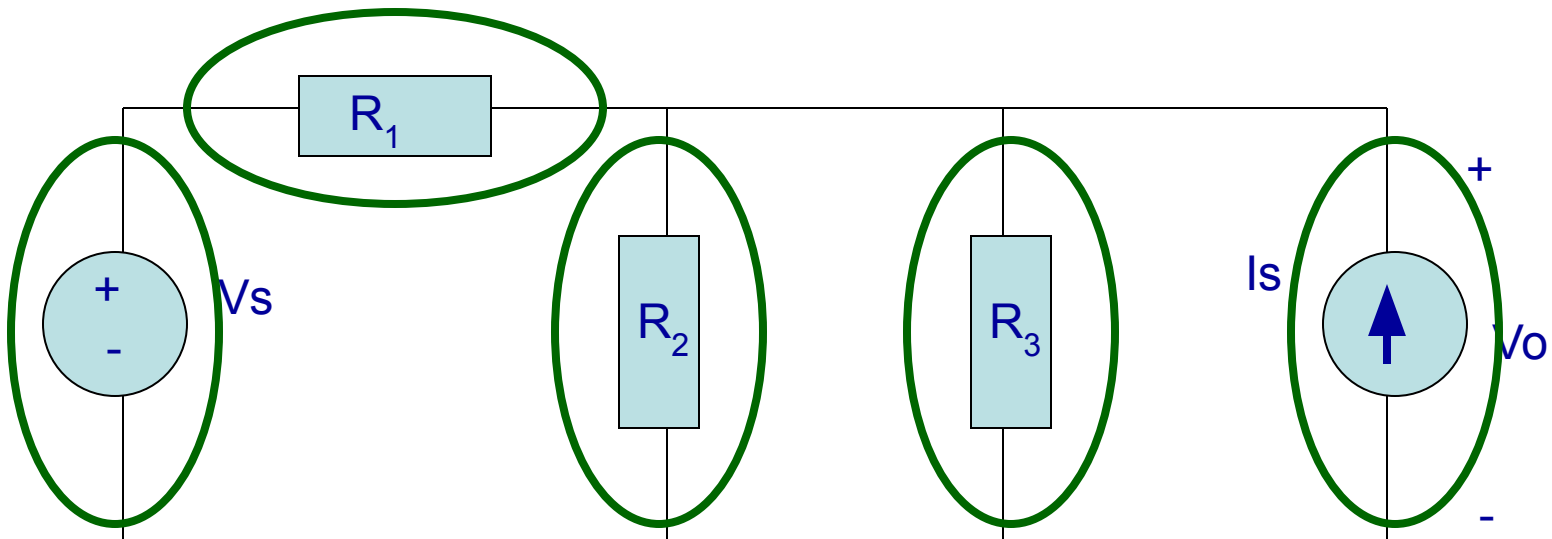

# Example

- Three Loops, if starting at node A

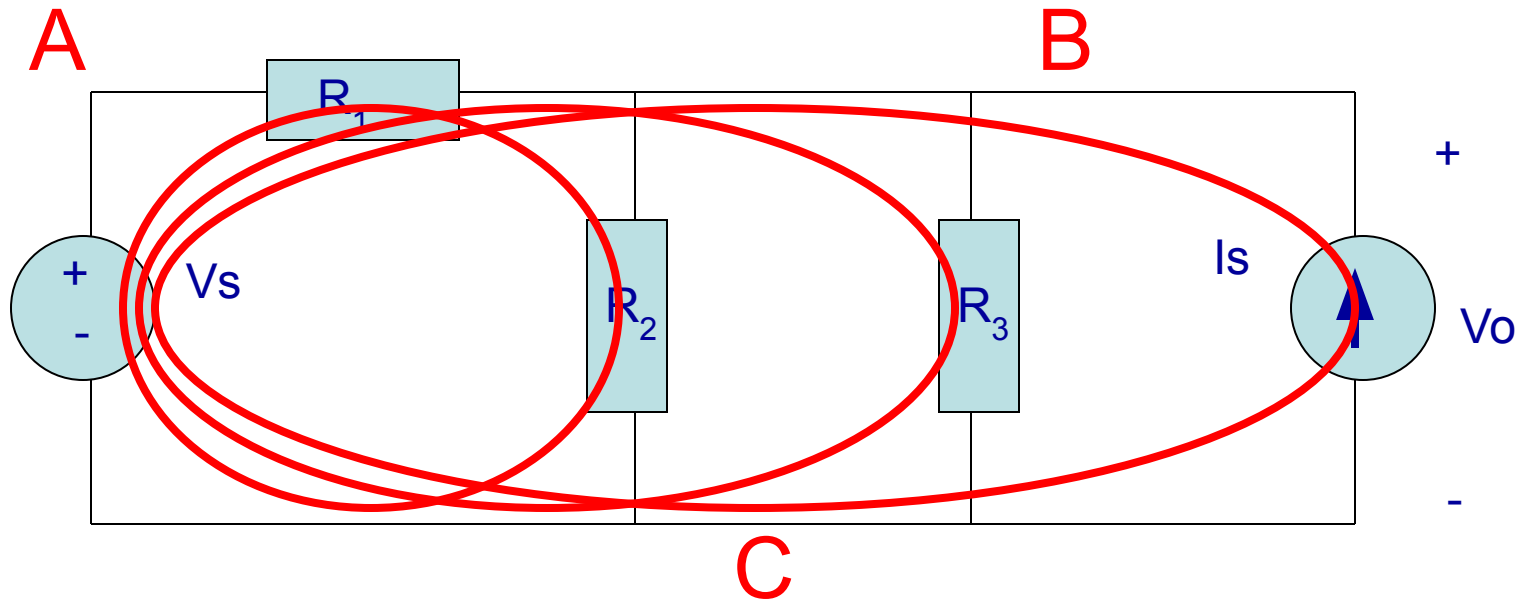


# Kirchoff's Voltage Law (KVL)

- The algebraic sum of voltages around each loop is zero
  - Beginning with one node, add voltages across each branch in the loop (if you encounter a + sign first) and subtract voltages (if you encounter a – sign first)
- $\Sigma \text{ voltage drops} - \Sigma \text{ voltage rises} = 0$
- Or  $\Sigma \text{ voltage drops} = \Sigma \text{ voltage rises}$
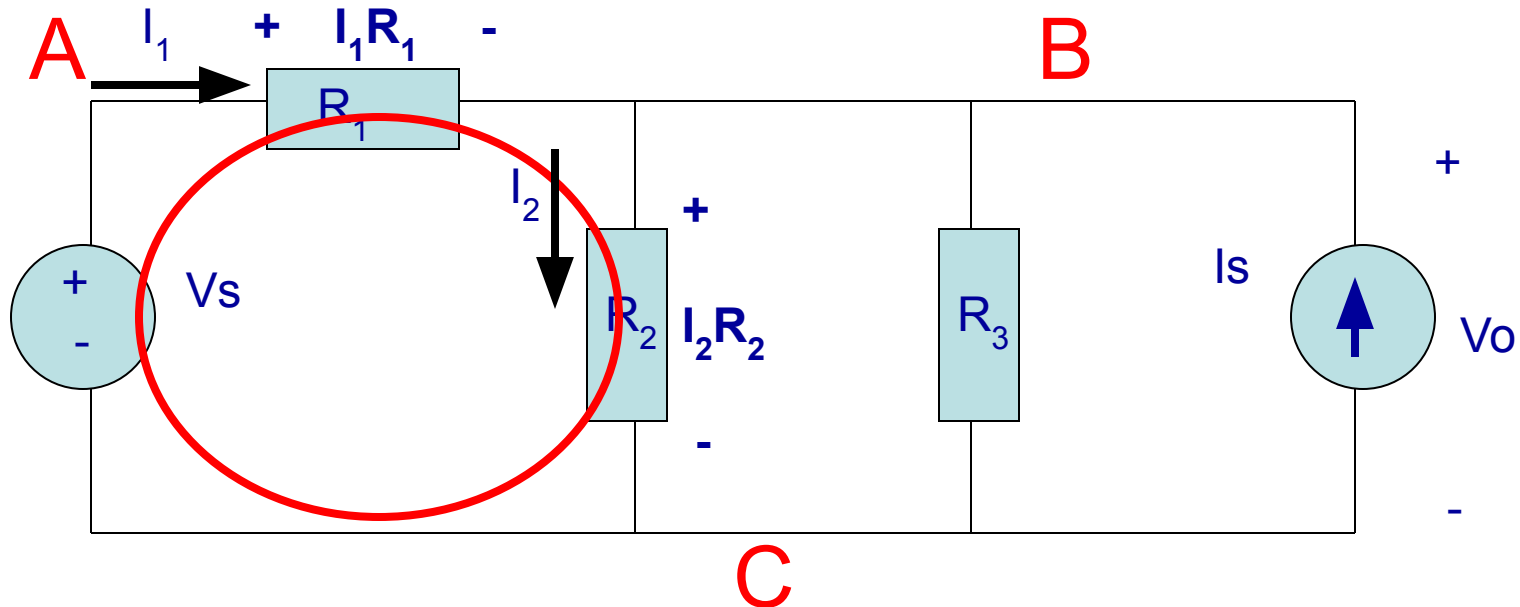
# Example

- Kirchoff's Voltage Law around 1<sup>st</sup> Loop




Assign current variables and directions

Use Ohm's law to assign voltages and polarities consistent with passive devices (current enters at the + side)


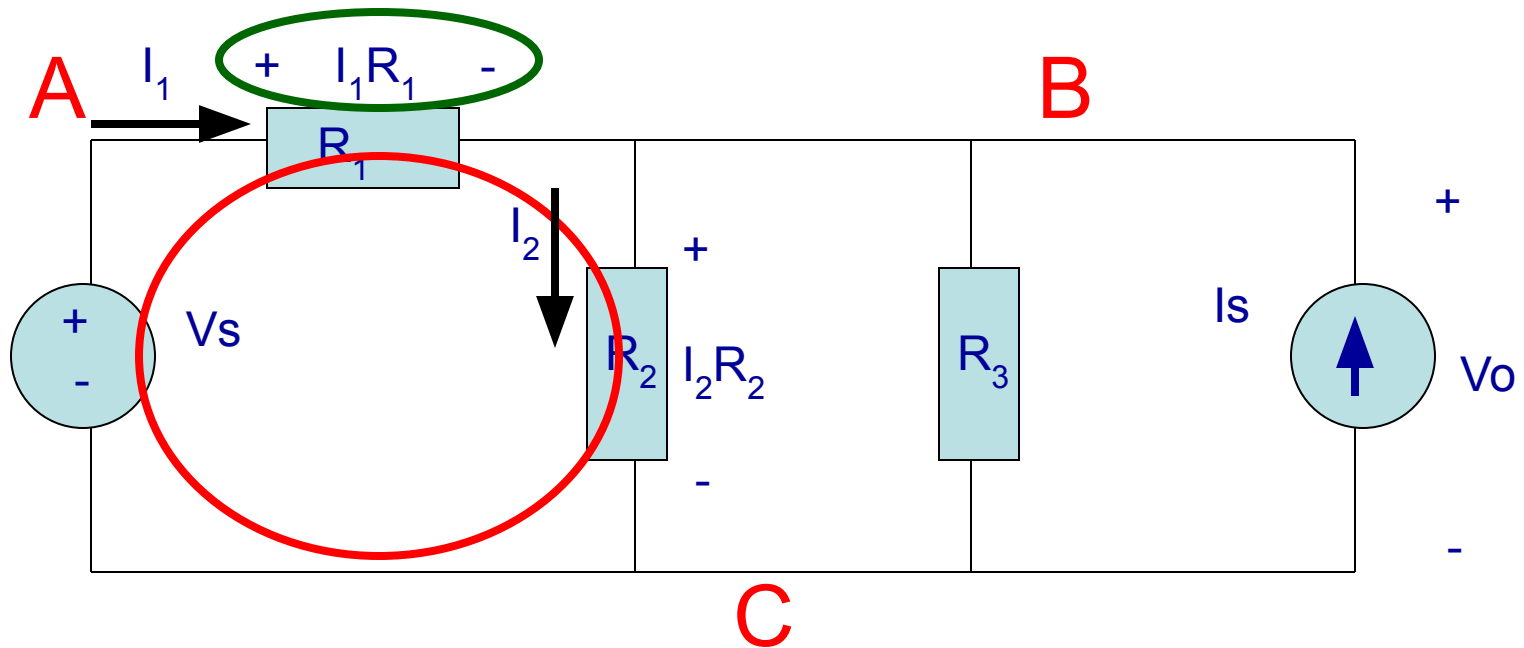
# Example


- Kirchoff's Voltage Law around 1<sup>st</sup> Loop



Starting at node A, add the 1<sup>st</sup> voltage drop:  $+ I_1 R_1$
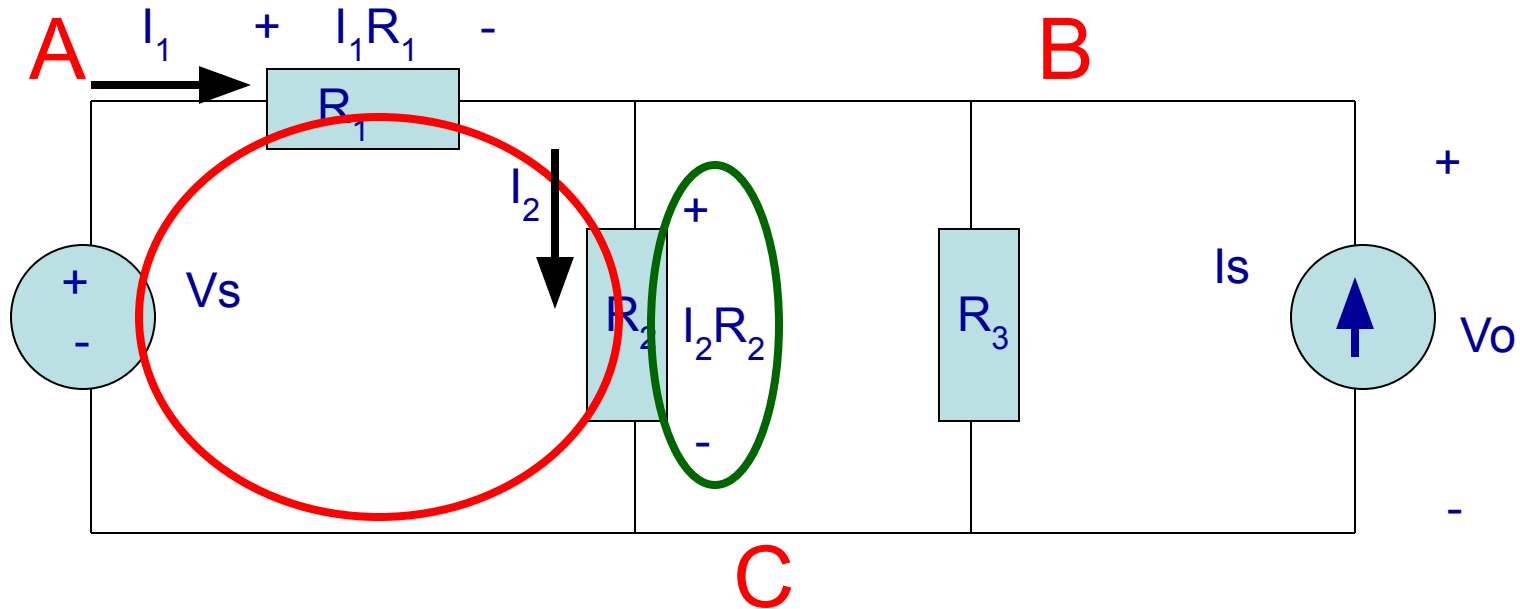
# Example


- Kirchoff's Voltage Law around 1<sup>st</sup> Loop



Add the voltage drop from B to C through  $R_2$ :  $+I_1R_1 + I_2R_2$
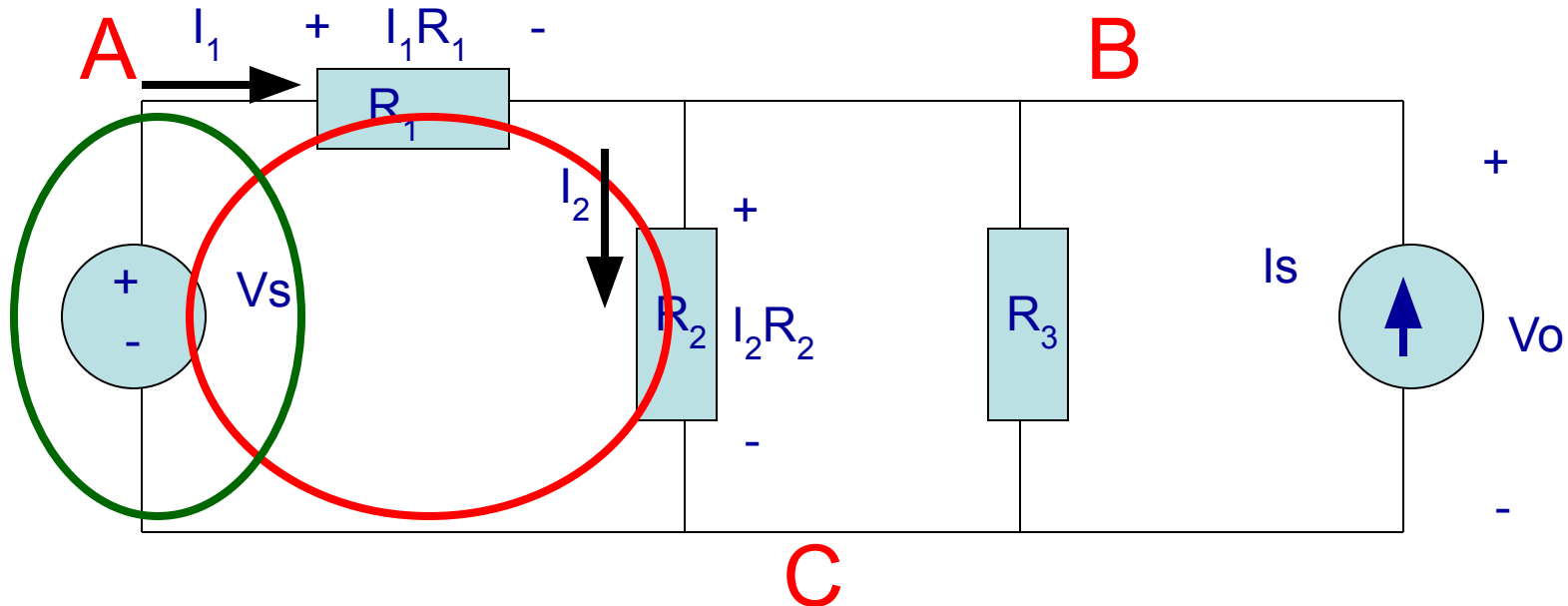
# Example

- Kirchoff's Voltage Law around 1<sup>st</sup> Loop




Subtract the voltage rise from C to A through  $V_s$ :  $+ I_1 R_1 + I_2 R_2 - V_s = 0$

Notice that the sign of each term matches the polarity encountered 1st

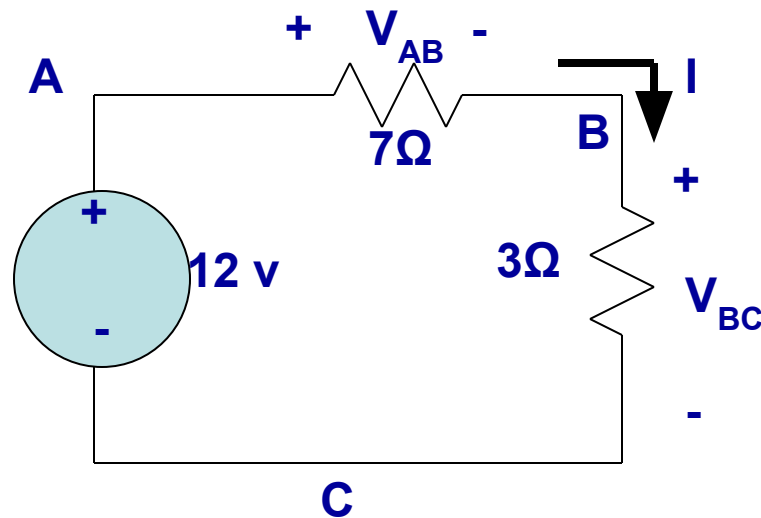
# Circuit Analysis

- When given a circuit with sources and resistors having fixed values, you can use Kirchhoff's two laws and Ohm's law to determine all branch voltages and currents



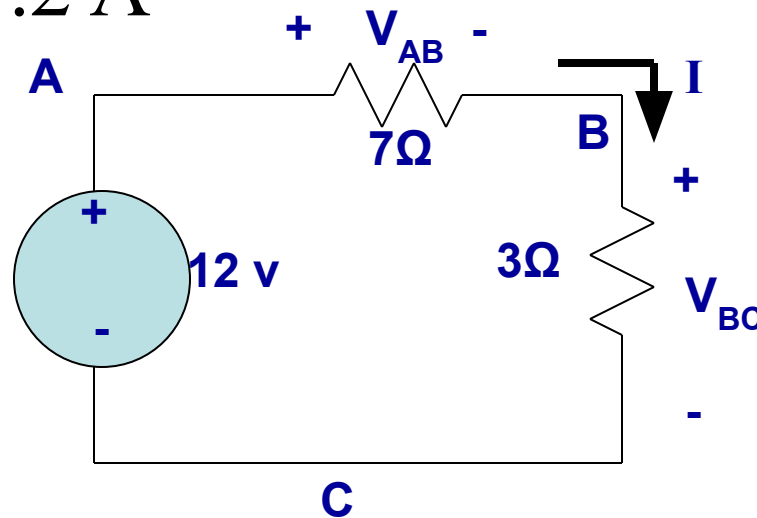
# Circuit Analysis

- By Ohm's law:  $V_{AB} = I \cdot 7\Omega$  and  $V_{BC} = I \cdot 3\Omega$
- By KVL:  $V_{AB} + V_{BC} - 12\text{ v} = 0$
- Substituting:  $I \cdot 7\Omega + I \cdot 3\Omega - 12\text{ v} = 0$
- Solving:  $I = 1.2\text{ A}$



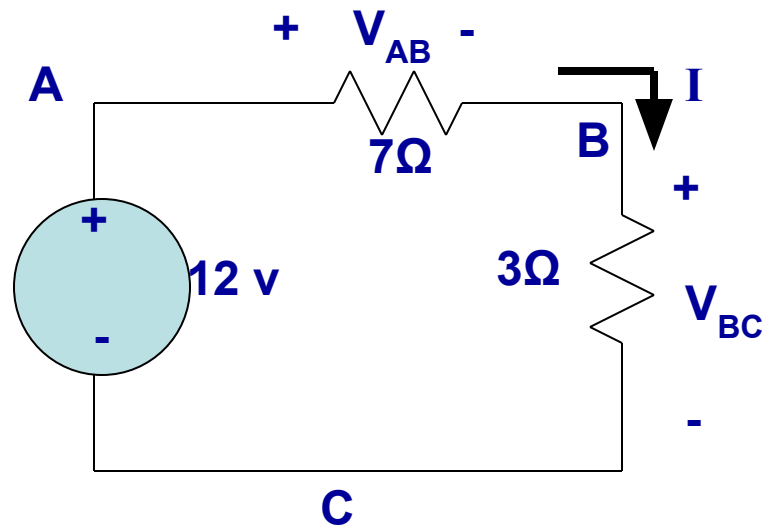
# Circuit Analysis

- Since  $V_{AB} = I \cdot 7\Omega$  and  $V_{BC} = I \cdot 3\Omega$
- And  $I = 1.2 \text{ A}$
- So  $V_{AB} = 8.4 \text{ v}$  and  $V_{BC} = 3.6 \text{ v}$



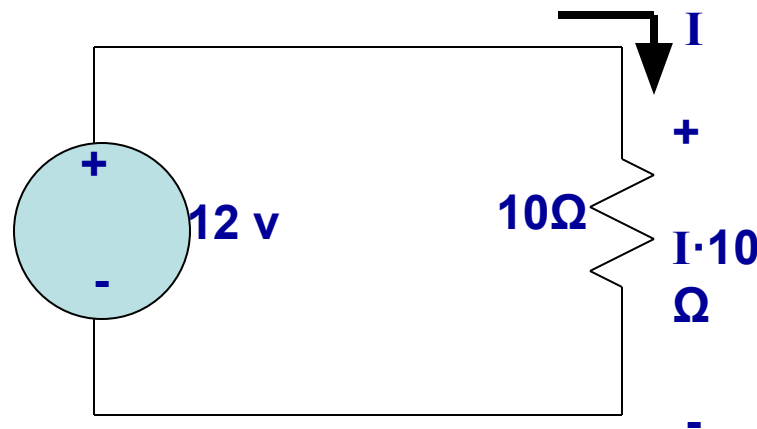
# Series Resistors

- KVL:  $+I \cdot 10\Omega - 12\text{ v} = 0$ , So  $I = 1.2\text{ A}$
- From the viewpoint of the source, the 7 and 3 ohm resistors in series are equivalent to the 10 ohms


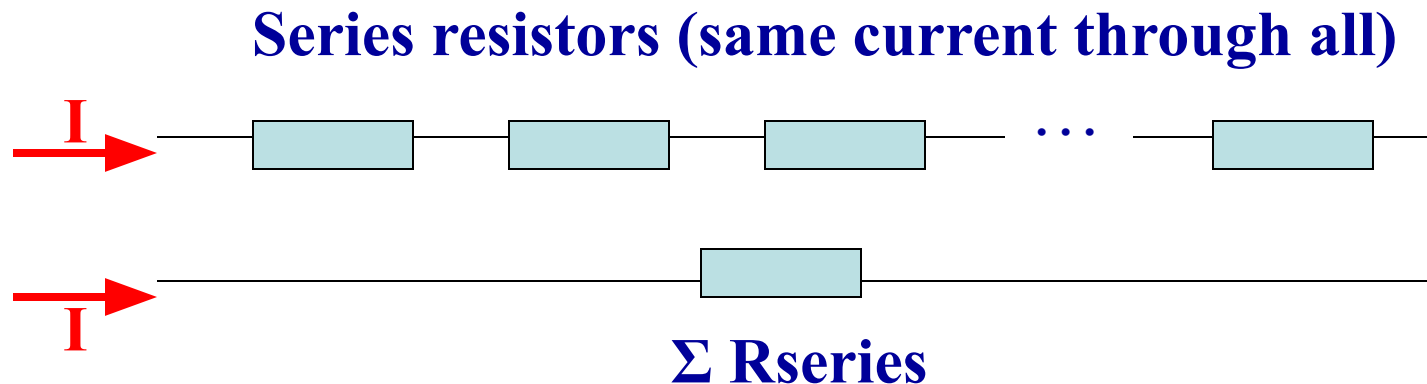
# Series Resistors

- To the rest of the circuit, series resistors can be replaced by an equivalent resistance equal to the sum of all resistors






# Kirchoff's Current Law (KCL)

- The algebraic sum of currents entering a node is zero
  - Add each branch current entering the node and subtract each branch current leaving the node
- $\sum \text{currents in} - \sum \text{currents out} = 0$
- Or  $\sum \text{currents in} = \sum \text{currents out}$

# Example


- Kirchoff's Current Law at B

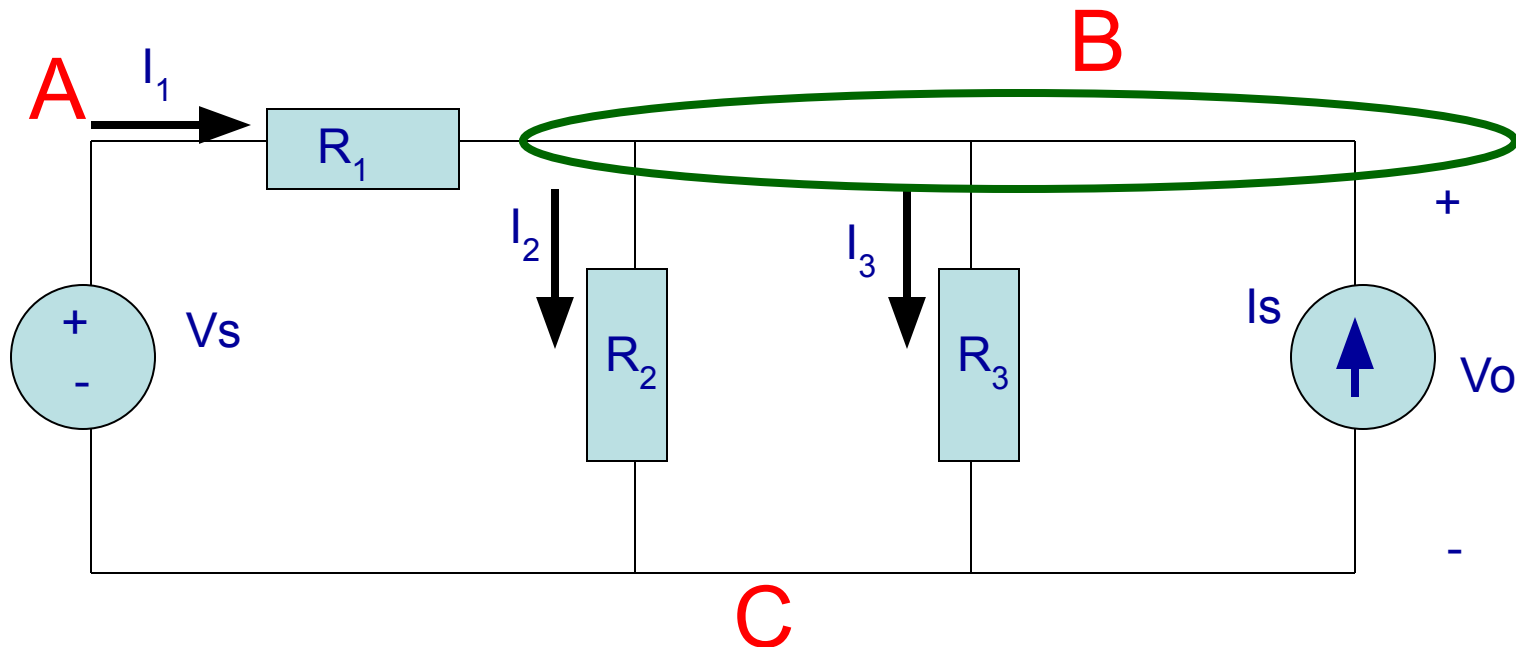

Assign current variables and directions

Add currents in, subtract currents out:  $I_1 - I_2 - I_3 + I_s = 0$

# Circuit Analysis

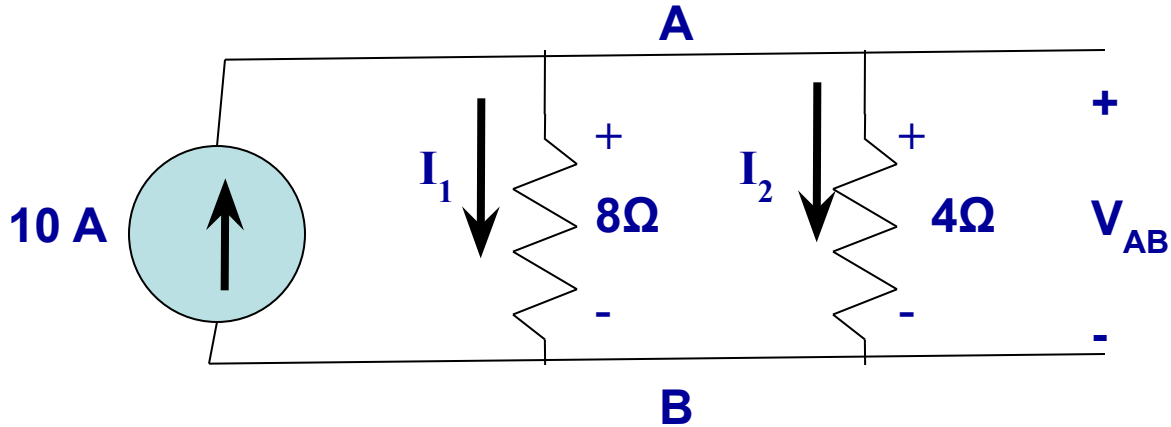

**By KVL:**  $-I_1 \cdot 8\Omega + I_2 \cdot 4\Omega = 0$

**Solving:**  $I_2 = 2 \cdot I_1$


**By KCL:**  $10\text{A} = I_1 + I_2$

**Substituting:**  $10\text{A} = I_1 + 2 \cdot I_1 = 3 \cdot I_1$

**So**  $I_1 = 3.33 \text{ A}$  **and**  $I_2 = 6.67 \text{ A}$

**And**  $V_{AB} = 26.33 \text{ volts}$


# Circuit Analysis

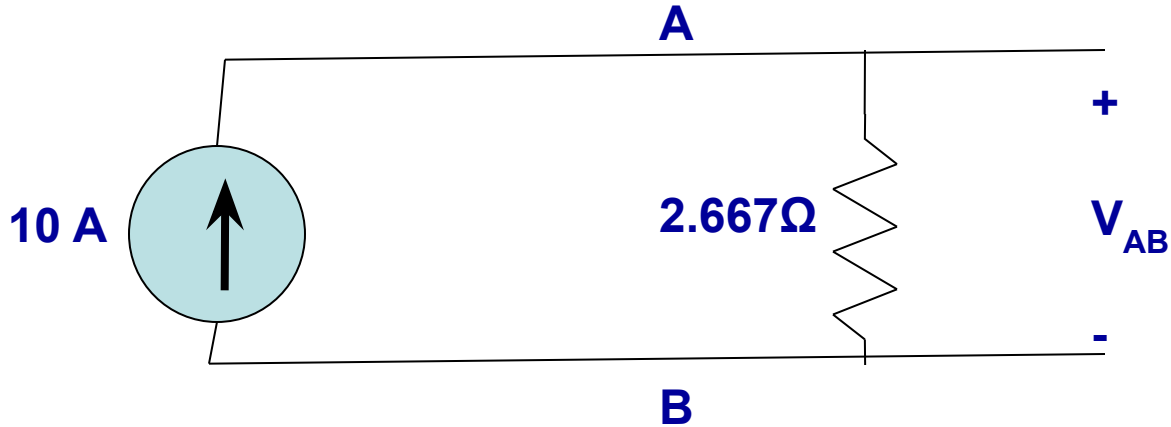

**By Ohm's Law:  $V_{AB} = 10\text{ A} \cdot 2.667\ \Omega$**   
**So  $V_{AB} = 26.67\text{ volts}$**


**Replacing two parallel resistors (8 and 4  $\Omega$ )  
by one equivalent one produces the same  
result from the viewpoint of the rest of the  
circuit.**

# Example Circuit

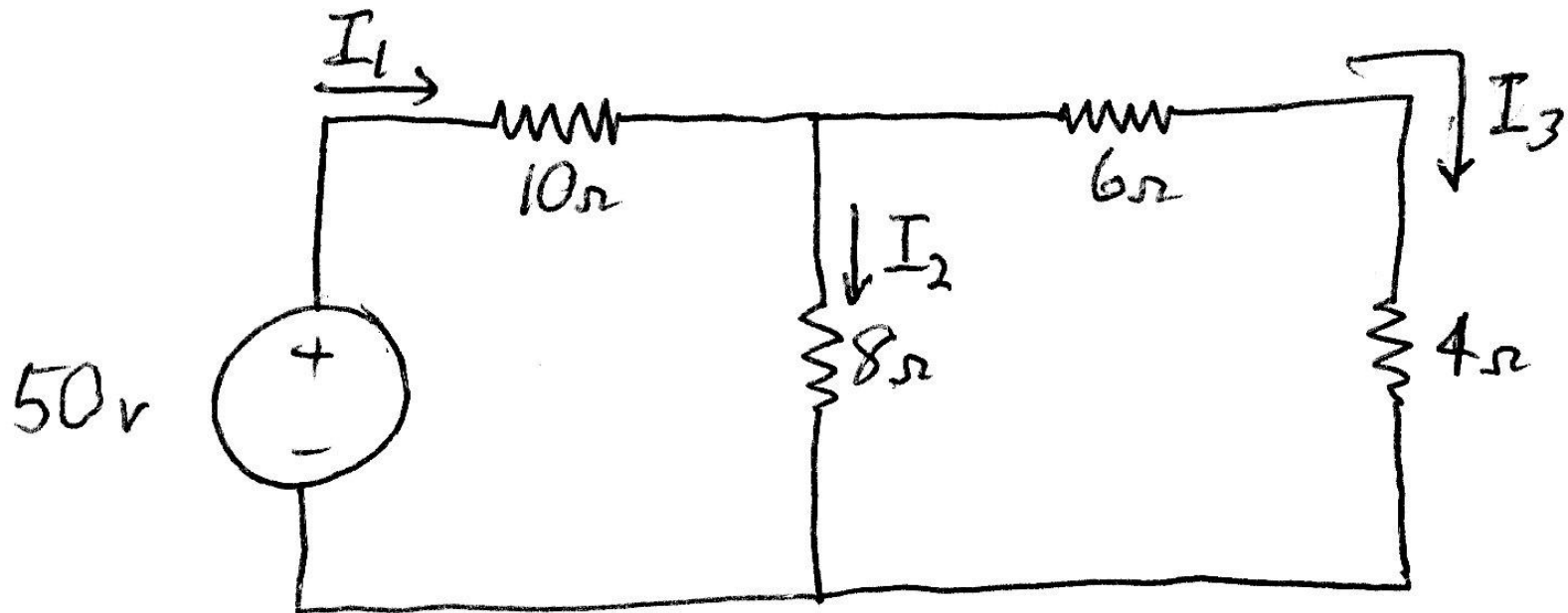


**Solve for the currents through each resistor  
And the voltages across each resistor**

# Example Circuit

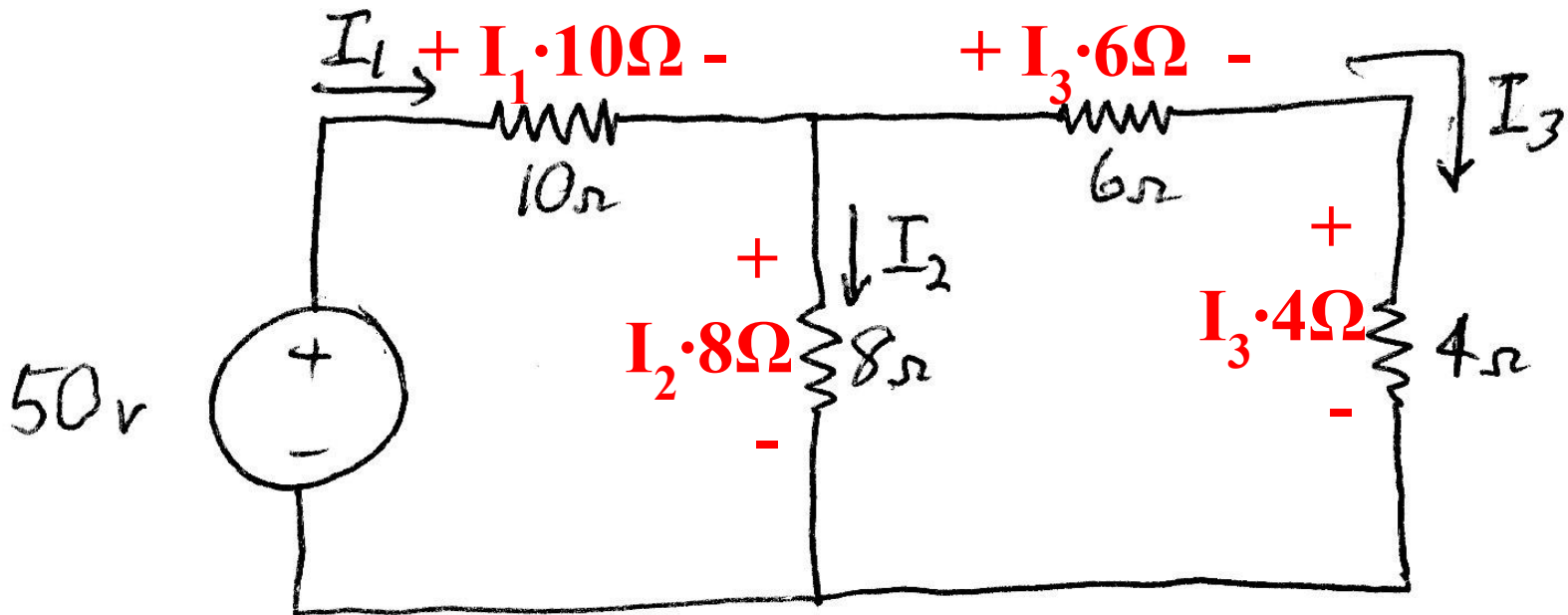

**Using Ohm's law, add polarities and expressions for each resistor voltage**


# Example Circuit

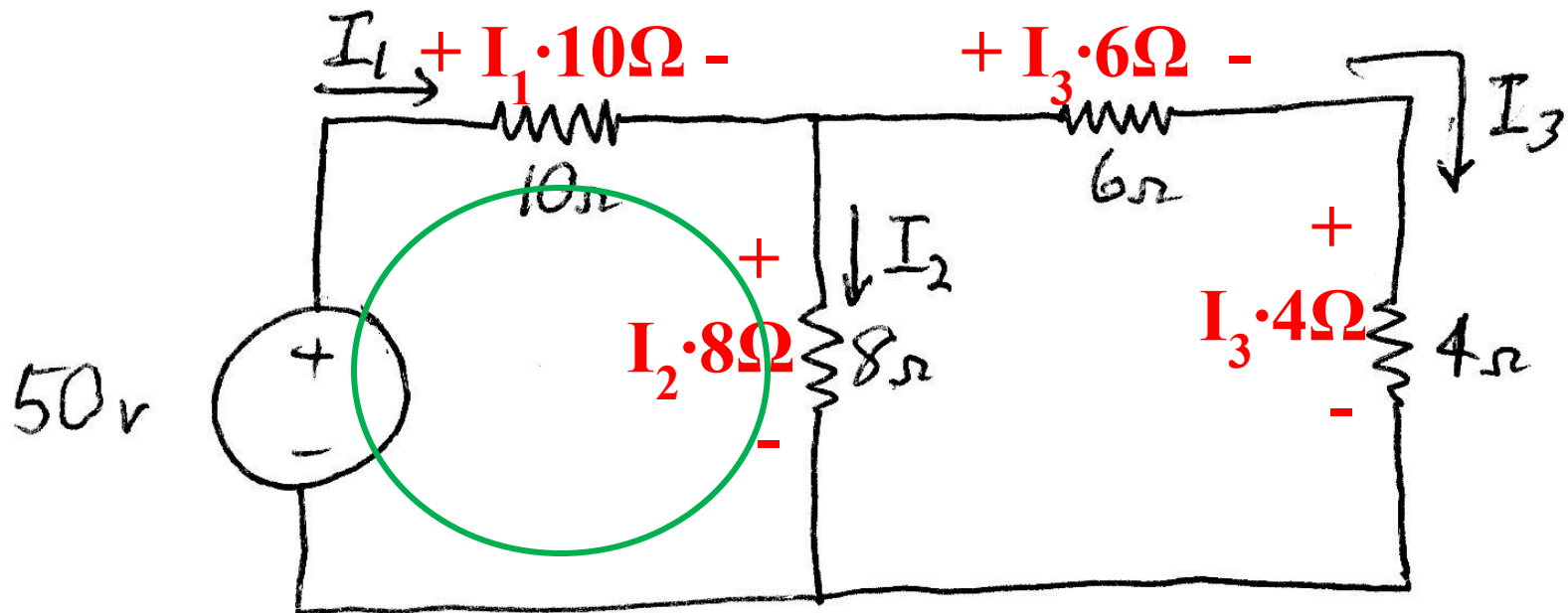

**Write 1<sup>st</sup> Kirchhoff's voltage law equation**

$$-50 \text{ v} + I_1 \cdot 10\Omega + I_2 \cdot 8\Omega = 0$$

# Example Circuit

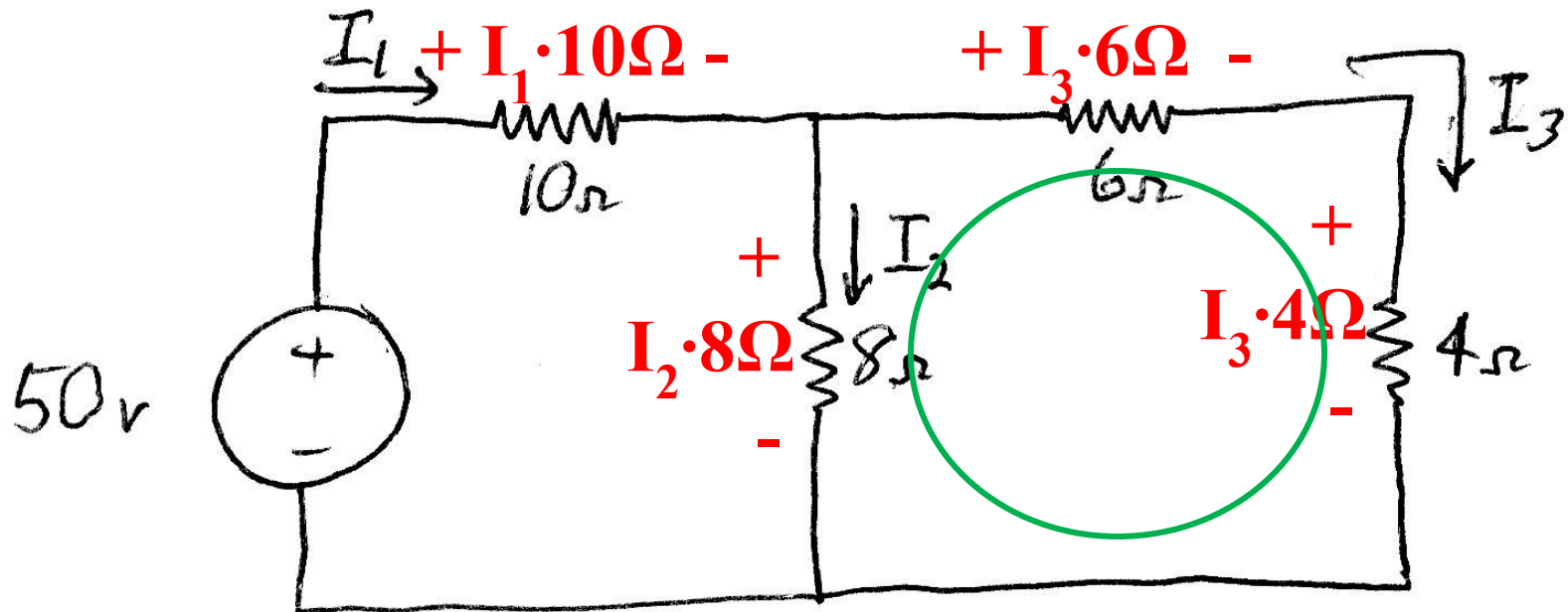


**Write 2<sup>nd</sup> Kirchhoff's voltage law equation**

$$-I_2 \cdot 8\Omega + I_3 \cdot 6\Omega + I_3 \cdot 4\Omega = 0$$

$$\text{or } I_2 = I_3 \cdot (6+4)/8 = 1.25 \cdot I_3$$



# Example Circuit

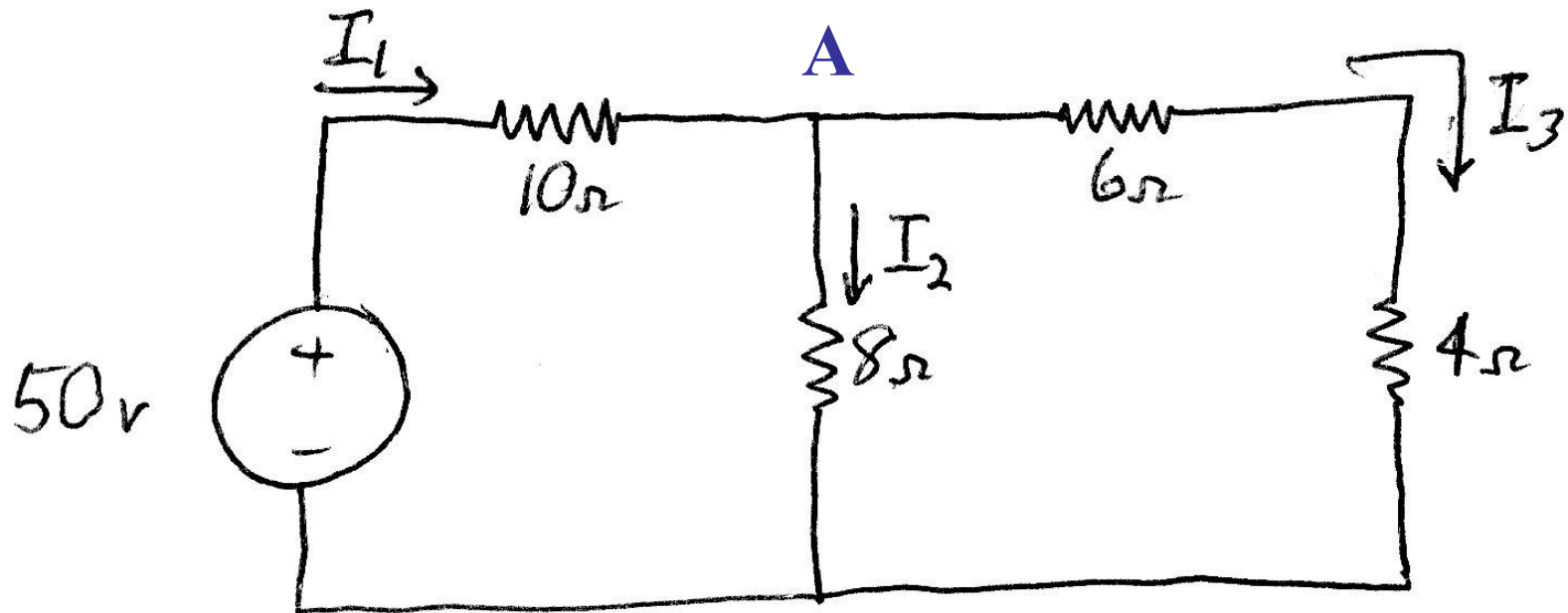

**Write Kirchhoff's current law equation at A**

$$+I_1 - I_2 - I_3 = 0$$

# Example Circuit

- We now have 3 equations in 3 unknowns, so we can solve for the currents through each resistor, that are used to find the voltage across each resistor
- Since  $I_1 - I_2 - I_3 = 0$ ,  $I_1 = I_2 + I_3$
- Substituting into the 1st KVL equation
$$-50 \text{ v} + (I_2 + I_3) \cdot 10\Omega + I_2 \cdot 8\Omega = 0$$
or  $I_2 \cdot 18 \Omega + I_3 \cdot 10 \Omega = 50 \text{ volts}$

# Example Circuit

- But from the 2<sup>nd</sup> KVL equation,  $I_2 = 1.25 \cdot I_3$
- Substituting into 1<sup>st</sup> KVL equation:

$$(1.25 \cdot I_3) \cdot 18 \, \Omega + I_3 \cdot 10 \, \Omega = 50 \text{ volts}$$

$$\text{Or: } I_3 \cdot 22.5 \, \Omega + I_3 \cdot 10 \, \Omega = 50 \text{ volts}$$

$$\text{Or: } I_3 \cdot 32.5 \, \Omega = 50 \text{ volts}$$


$$\text{Or: } I_3 = 50 \text{ volts} / 32.5 \, \Omega$$

$$\text{Or: } I_3 = 1.538 \text{ amps}$$

# Example Circuit


- Since  $I_3 = 1.538$  amps  
 $I_2 = 1.25 \cdot I_3 = 1.923$  amps
- Since  $I_1 = I_2 + I_3$ ,  $I_1 = 3.461$  amps
- The voltages across the resistors:  
 $I_1 \cdot 10\Omega = 34.61$  volts  
 $I_2 \cdot 8\Omega = 15.38$  volts  
 $I_3 \cdot 6\Omega = 9.23$  volts  
 $I_3 \cdot 4\Omega = 6.15$  volts

# Example Circuit

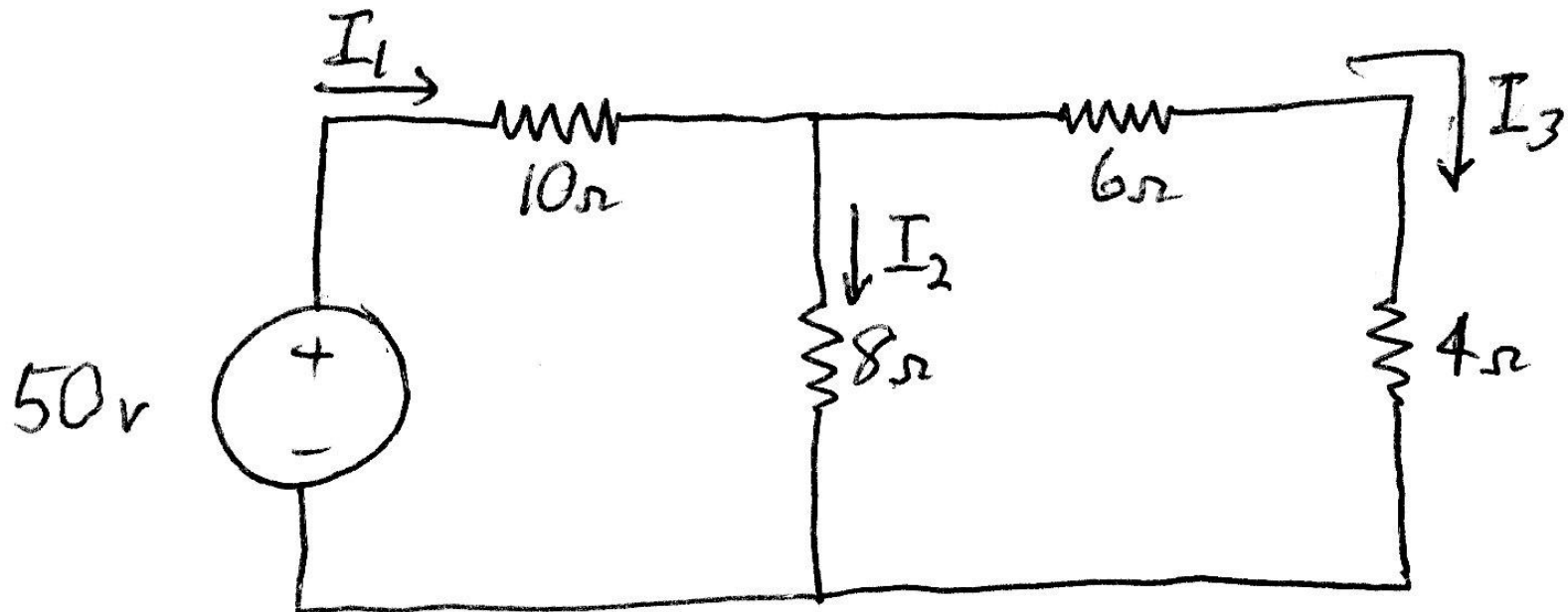


**Solve for the currents through each resistor  
And the voltages across each resistor using  
Series and parallel simplification.**

# Example Circuit

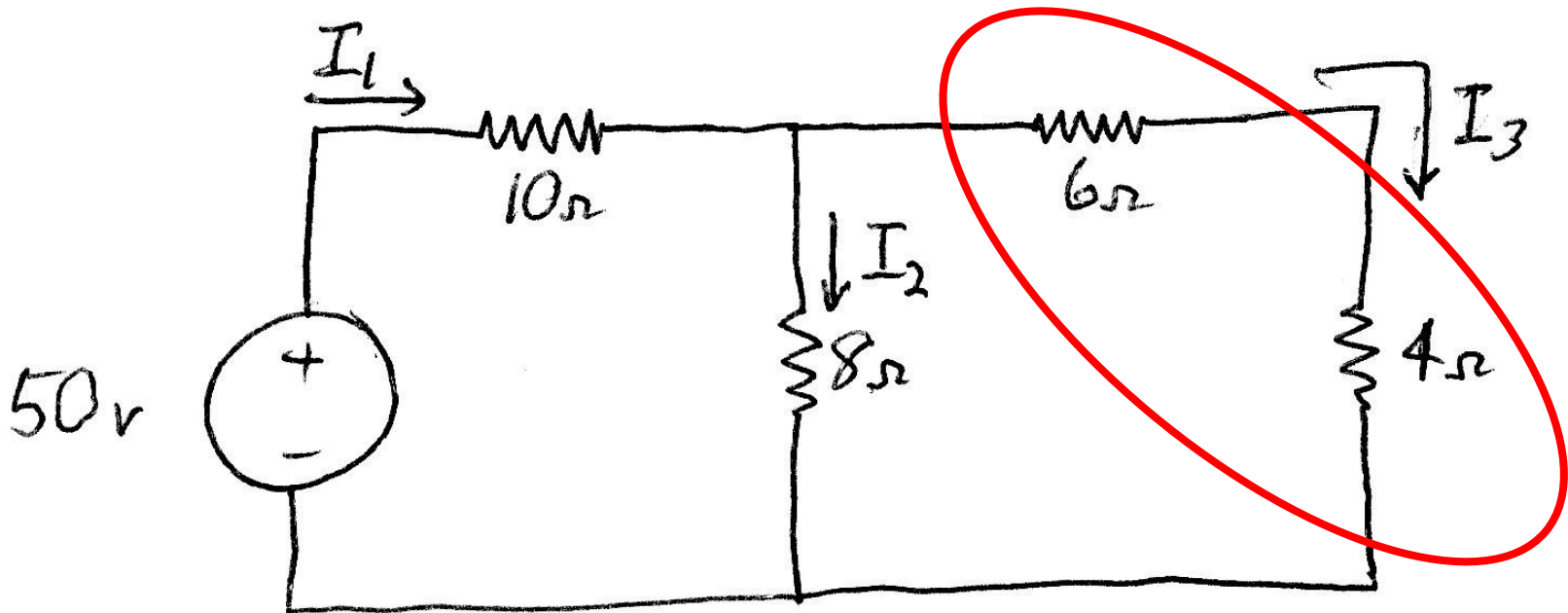


**The 6 and 4 ohm resistors are in series, so are combined into  $6+4 = 10\Omega$**

# Example Circuit

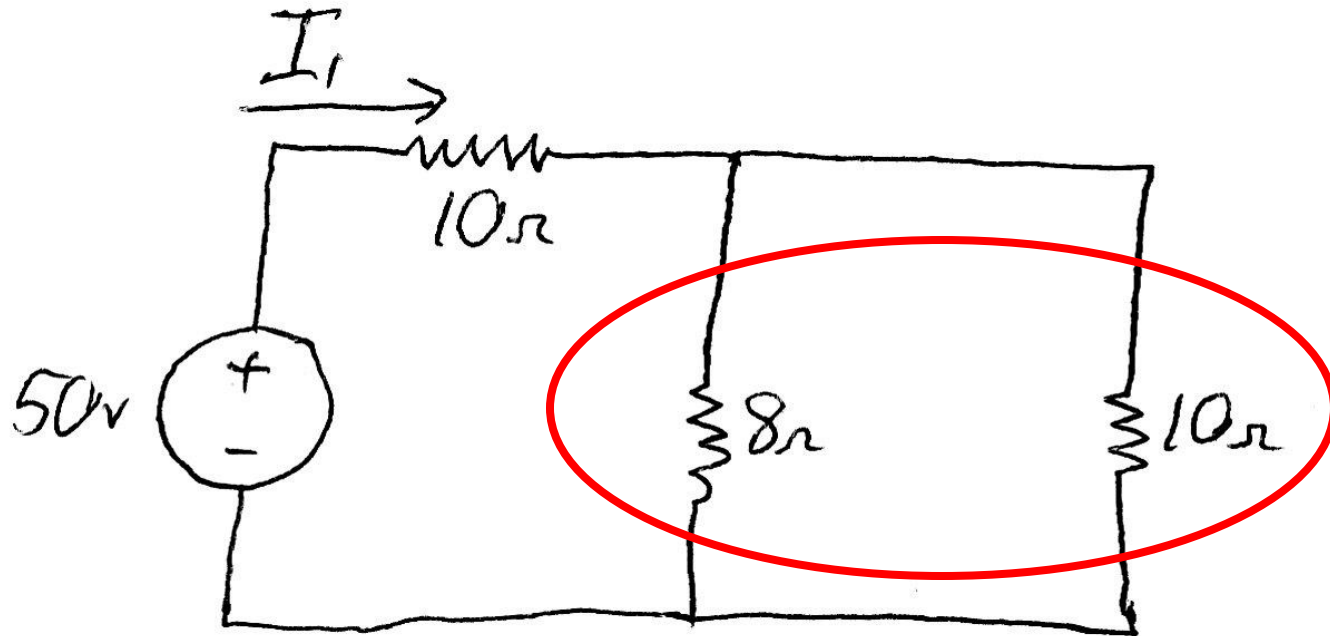

**The 8 and 10 ohm resistors are in parallel, so are combined into  $8 \cdot 10 / (8 + 10) = 14.4 \Omega$**


# Example Circuit

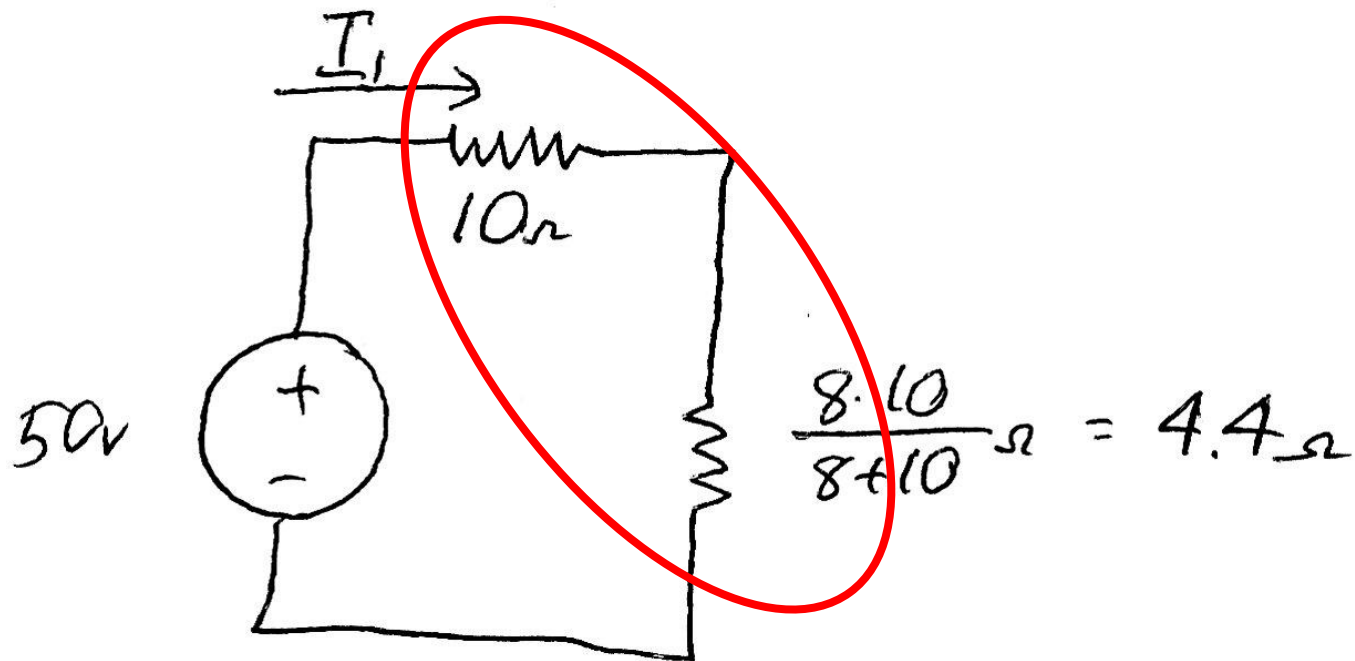

**The 10 and 4.4 ohm resistors are in series, so are combined into  $10 + 4 = 14.4\Omega$**




# Example Circuit

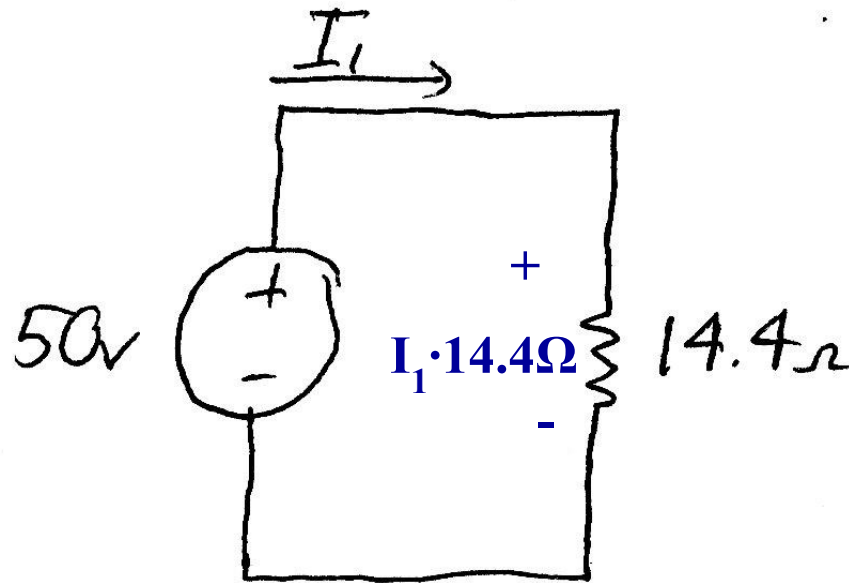

**Writing KVL,  $I_1 \cdot 14.4\Omega - 50 \text{ v} = 0$**

**Or  $I_1 = 50 \text{ v} / 14.4\Omega = 3.46 \text{ A}$**


# Example Circuit

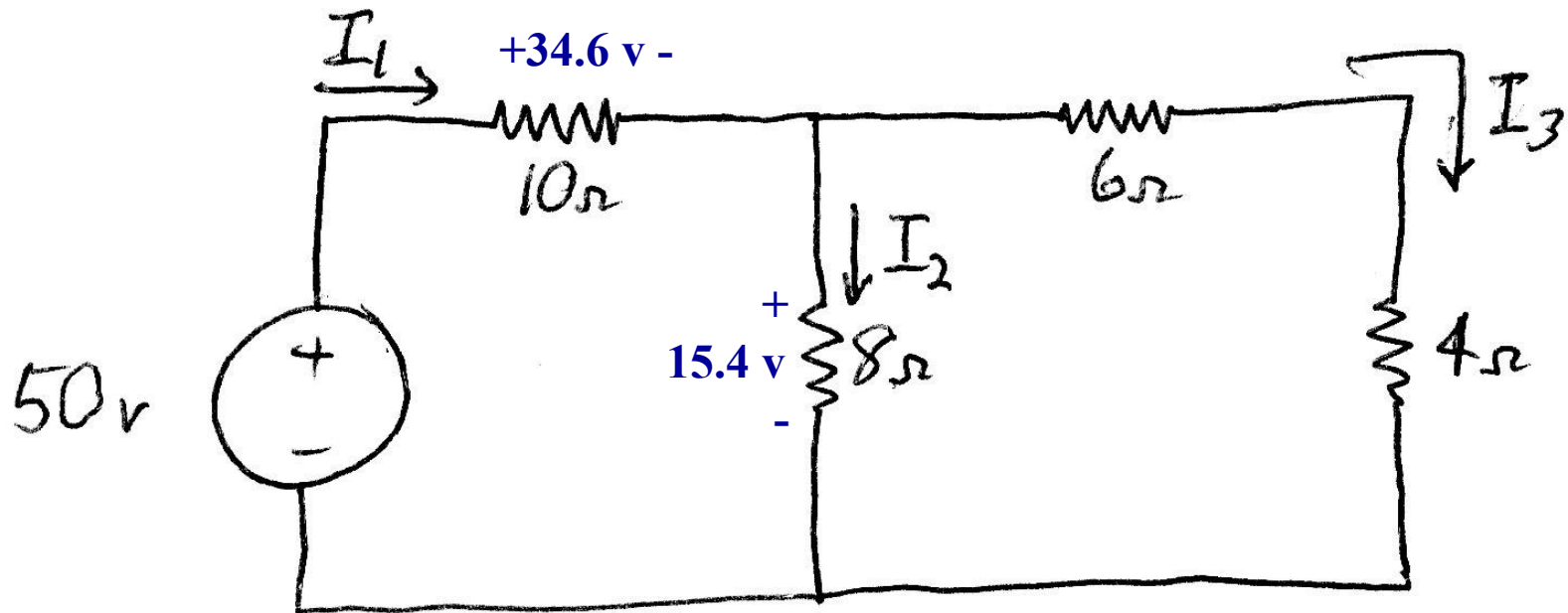

If  $I_1 = 3.46 \text{ A}$ , then  $I_1 \cdot 10 \Omega = 34.6 \text{ v}$

So the voltage across the  $8 \Omega = 15.4 \text{ v}$

# Example Circuit

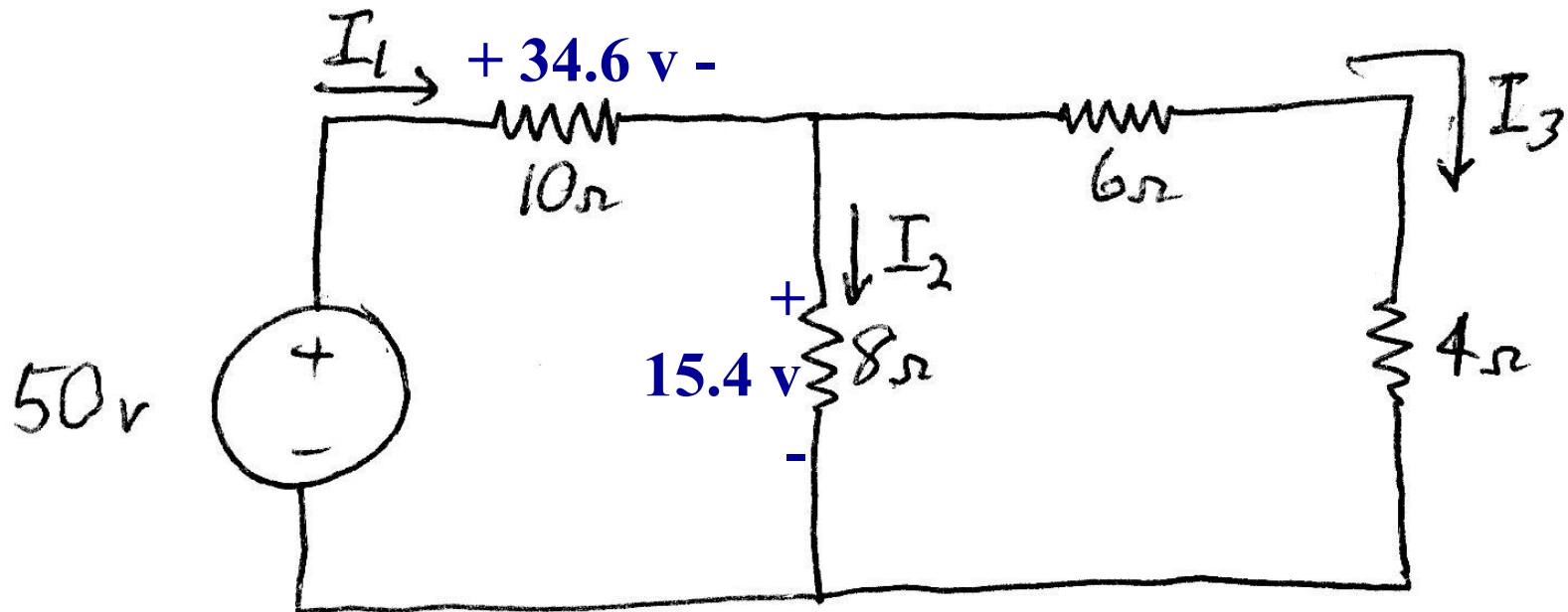

If  $I_2 \cdot 8 \, \Omega = 15.4 \, \text{v}$ , then  $I_2 = 15.4/8 = 1.93 \, \text{A}$

By KCL,  $I_1 - I_2 - I_3 = 0$ , so  $I_3 = I_1 - I_2 = 1.53 \, \text{A}$